

**ELL201**

**Experiment 6,7**  
**Lab Reports**

**Name: Raunak Jain**


**Entry Number: 2019MT10719**

# Experiment 6
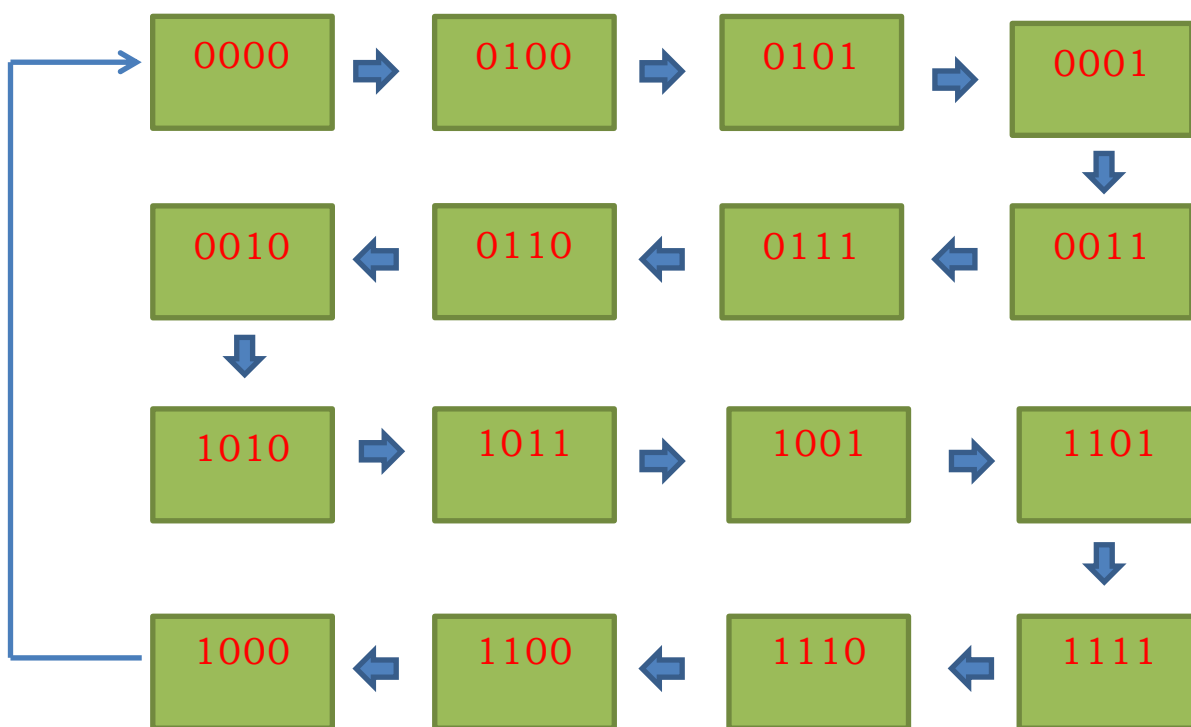
## 1. Synchronous 4-bit Gray-Code Counter:

- Made counter :

0->4->5->1->3->7->6->2->10->11->9->13->15->14->12->8->0.



**State Diagram**

**State Table:**

$A_n$	$B_n$	$C_n$	$D_n$	$A_{n+1}$	$B_{n+1}$	$C_{n+1}$	$D_{n+1}$
0	0	0	0	0	1	0	0
0	0	0	1	0	0	1	1
0	0	1	0	1	0	1	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	1
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	0	1	1
1	0	1	1	1	0	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	1	1	1
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0

- Since, it is a 4-bit counter, so we require **4 SR Flip-Flops**.

- **Values assigned to the inputs of Flip-Flops:**

A	B	C	D	S <sub>A</sub>	R <sub>A</sub>	S <sub>B</sub>	R <sub>B</sub>	S <sub>C</sub>	R <sub>C</sub>	S <sub>D</sub>	R <sub>D</sub>
0	0	0	0	0	X	1	0	0	X	0	X
0	0	0	1	0	X	0	X	1	0	X	0
0	0	1	0	1	0	0	X	X	0	0	X
0	0	1	1	0	X	1	0	X	0	X	0
0	1	0	0	0	X	X	0	0	X	1	0
0	1	0	1	0	X	0	1	0	X	X	0
0	1	1	0	0	X	0	1	X	0	0	X
0	1	1	1	0	X	X	0	X	0	0	1
1	0	0	0	0	1	0	X	0	X	0	X
1	0	0	1	X	0	1	0	0	X	X	0
1	0	1	0	X	0	0	X	X	0	1	0
1	0	1	1	X	0	0	X	0	1	X	0
1	1	0	0	X	0	0	1	0	X	0	X
1	1	0	1	X	0	X	0	1	0	X	0
1	1	1	0	X	0	X	0	0	1	0	X
1	1	1	1	X	0	X	0	X	0	0	1

- ❖ S<sub>A</sub> and R<sub>A</sub> are inputs of Flip-Flop A (Outputs: A and A')
- ❖ S<sub>B</sub> and R<sub>B</sub> are inputs of Flip-Flop B (Outputs: B and B')
- ❖ S<sub>C</sub> and R<sub>C</sub> are inputs of Flip-Flop C (Outputs: C and C')
- ❖ S<sub>D</sub> and R<sub>D</sub> are inputs of Flip-Flop D (Outputs: D and D')

- Karnaugh Maps:**

AB \ CD	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	X	X	X	X
10	0	X	X	X

**S<sub>A</sub>**

AB \ CD	00	01	11	10
00	X	X	X	0
01	X	X	X	X
11	0	0	0	0
10	1	0	0	0

**R<sub>A</sub>**

AB \ CD	00	01	11	10
00	1	0	1	0
01	X	0	X	0
11	0	X	X	X
10	0	1	0	0

**S<sub>B</sub>**

AB \ CD	00	01	11	10
00	0	X	0	X
01	0	1	0	1
11	1	0	0	0
10	X	0	X	X

**R<sub>B</sub>**

AB \ CD	00	01	11	10
00	0	1	X	X
01	0	0	X	X
11	0	1	X	0
10	0	0	0	X

**S<sub>C</sub>**

AB \ CD	00	01	11	10
00	X	0	0	0
01	X	X	0	0
11	X	0	0	1
10	X	X	1	0

**R<sub>C</sub>**

AB \ CD	00	01	11	10
00	0	X	X	0
01	1	X	0	0
11	0	X	0	0
10	0	X	X	1

**S<sub>D</sub>**

AB \ CD	00	01	11	10
00	X	0	0	X
01	0	0	1	X
11	X	0	1	X
10	X	0	0	0

**R<sub>D</sub>**

- **Minimized Expressions for inputs are:**

❖ For SR Flip-Flop which gives A,A' as outputs:

$$\mathbf{S_A = B'CD' \text{ and } R_A = B'C'D'}$$

❖ For SR Flip-Flop which gives B,B' as outputs:

$$\mathbf{S_B = A'C'D'+A'CD+AC'D \text{ and } R_B = AC'D'+A'C'D+A'CD'}$$

❖ For SR Flip-Flop which gives C,C' as outputs:

$$\mathbf{S_C = A'B'D+ABD \text{ and } R_C = AB'D+ABD'}$$

❖ For SR Flip-Flop which gives D,D' as outputs:

$$\mathbf{S_D = A'BC'+AB'C \text{ and } R_D = BC}$$

- **Verilog Code:**

- ❖ Generating Counter code:

```
module graycode(A,B,C,D,Acomp,Bcomp,Ccomp,Dcomp,clk,rst);

input clk,rst;
output A,B,C,D,Acomp,Bcomp,Ccomp,Dcomp;

wire SA,RA,SB1,SB2,SB3,SB,RB1,RB2,RB3,RB,SC1,SC2,SC,RC1,RC2,RC,SD1,SD2,SD,RD;

and(SA,Bcomp,C,Dcomp);
and(RA,Bcomp,Ccomp,Dcomp);
and(SB1,Acomp,Ccomp,Dcomp);
and(SB2,Acomp,C,D);
and(SB3,A,Ccomp,D);
or(SB,SB1,SB2,SB3);
and(RB1,A,Ccomp,Dcomp);
and(RB2,Acomp,Ccomp,D);
and(RB3,Acomp,C,Dcomp);
or(RB,RB1,RB2,RB3);
and(SC1,Acomp,Bcomp,D);
and(SC2,A,B,D);
or(SC,SC1,SC2);
and(RC1,A,Bcomp,D);
and(RC2,A,B,Dcomp);
or(RC,RC1,RC2);
and(SD1,Acomp,B,Ccomp);
and(SD2,A,Bcomp,C);
or(SD,SD1,SD2);
and(RD,B,C);

SRFlipFlop SRA(A,Acomp,rst,SA,RA,clk);
SRFlipFlop SRB(B,Bcomp,rst,SB,RB,clk);
SRFlipFlop SRC(C,Ccomp,rst,SC,RC,clk);
SRFlipFlop SRD(D,Dcomp,rst,SD,RD,clk);

endmodule

module SRFlipFlop(Q,Qcomp,rst,S,R,clk);

input S,R,rst,clk;
output reg Q,Qcomp;

always @(clk | rst)
begin
  if(rst == 1)
  begin
    Q = 0;
    Qcomp = 1;
  end
end

always @(posedge clk)
begin
  Q = S | (~R&Q);
  Qcomp = ~Q;
end

endmodule
```

## ❖ Testing Code:

```
module test_graycode;

reg clk,rst;
wire A,Acomp,B,Bcomp,C,Ccomp,D,Dcomp;

graycode DUT(A,B,C,D,Acomp,Bcomp,Ccomp,Dcomp,clk,rst);


always #10 clk = ~clk;

initial
begin
    $dumpfile("graycode.vcd");
    $dumpvars(0,test_graycode);
    $monitor ($time," %b%b%b%b", A, B, C, D);
    clk = 0;
    rst = 1;
    #2; rst = 0;
    repeat(20) @(posedge clk);
    $finish;
end

endmodule
```
 
## ❖ Output:

```
C:\Users\Raunak\Desktop\ELL201 Verilog>vvp model
VCD info: dumpfile graycode.vcd opened for output.
    0 0000
   10 0100
   30 0101
   50 0001
   70 0011
   90 0111
  110 0110
  130 0010
  150 1010
  170 1011
  190 1001
  210 1101
  230 1111
  250 1110
  270 1100
  290 1000
  310 0000
  330 0100
  350 0101
  370 0001
test_graycode.v:19: $finish called at 390 (1s)
  390 0011
```





## 2. Synchronous Ring Counter:

- We require **4 D Flip-Flops** as there are 4 outputs ( $Q_0, Q_1, Q_2, Q_3$ ).
- **Values assigned to the inputs:**

$Q_0$	$Q_1$	$Q_2$	$Q_3$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	0	0	X	X	X	X
0	0	0	1	0	0	0	1
0	0	1	0	1	0	0	1
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0
1	0	0	1	0	0	1	1
1	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	0
1	1	0	1	0	1	1	1
1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	0

- **Karnaugh Maps:**

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

**D<sub>0</sub>**

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

**D<sub>1</sub>**

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

**D<sub>2</sub>**

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	X	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

**D<sub>3</sub>**

**On Minimizing Input Expression using Karnaugh Map:**

- ❖  $D_0 = Q_1$
- ❖  $D_1 = Q_2$
- ❖  $D_2 = Q_3$
- ❖  $D_3 = Q_1'Q_0 + Q_1Q_0' = Q_1 \text{ xor } Q_0$

- My Entry Number is 2019MT10719 and hence, X4 = 9 which is 1001. So, my counter will start from 1001 i.e.  $Q_3 = 1$ ,  $Q_2 = 0$ ,  $Q_1 = 0$  and  $Q_0 = 1$ .

- **Verilog Code:**

❖ Ring counter Code:

```
module ringcounter(Q0,Q1,Q2,Q3,Q0comp,Q1comp,Q2comp,Q3comp,clk,rst);

input clk,rst;
output Q0,Q1,Q2,Q3,Q0comp,Q1comp,Q2comp,Q3comp;
wire D0,D1,D2,D3,a,b;

assign a = 1;
assign b = 0;

buf(D0,Q1);
buf(D1,Q2);
buf(D2,Q3);
xor(D3,Q0,Q1);

DFlipFlop DQ0(Q0,Q0comp,D0,clk,rst,a,b);
DFlipFlop DQ1(Q1,Q1comp,D1,clk,rst,b,a);
DFlipFlop DQ2(Q2,Q2comp,D2,clk,rst,b,a);
DFlipFlop DQ3(Q3,Q3comp,D3,clk,rst,a,b);

endmodule

module DFlipFlop(Q,Qcomp,D,clk,rst,a,b);

input D,clk,rst,a,b;
output reg Q,Qcomp;

always @(clk | rst)
begin
    if(rst == 1)
        begin
            Q = a;
            Qcomp = b;
        end
    end
end

always @(posedge clk)
begin
    Q = D;
    Qcomp = ~Q;
end

endmodule
```

## ❖ Tester Code:

```
module test_ringcounter;

reg clk,rst;
wire Q0,Q0comp,Q1,Q1comp,Q2,Q2comp,Q3,Q3comp;

ringcounter DUT(Q0,Q1,Q2,Q3,Q0comp,Q1comp,Q2comp,Q3comp,clk,rst);


always #10 clk = ~clk;

initial
begin
  $dumpfile("ringcounter.vcd");
  $dumpvars(0,test_ringcounter);
  $monitor ($time," %b%b%b%b", Q3, Q2, Q1, Q0);
  clk = 0;
  rst = 1;
  #2; rst = 0;
  repeat(20) @(posedge clk);
  $finish;
end

endmodule
```
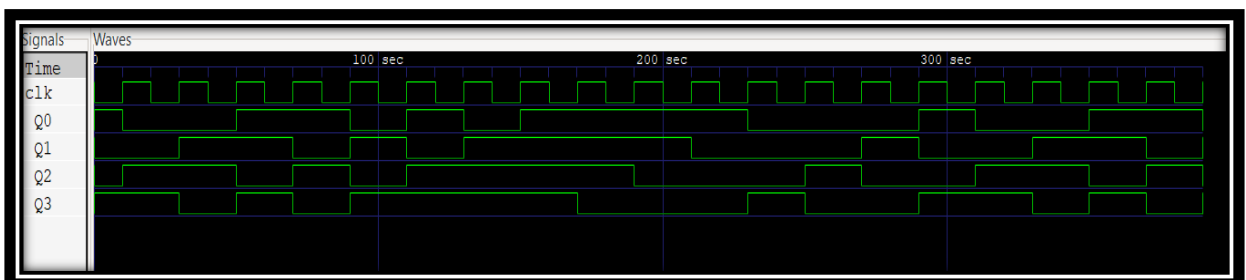
## ❖ Output:

```
C:\Users\Raunak\Desktop\ELL201 Verilog>vvp model
VCD info: dumpfile ringcounter.vcd opened for output.
   0 1001
  10 1100
  30 0110
  50 1011
  70 0101
  90 1010
 110 1101
 130 1110
 150 1111
 170 0111
 190 0011
 210 0001
 230 1000
 250 0100
 270 0010
 290 1001
 310 1100
 330 0110
 350 1011
 370 0101
test_ringcounter.v:19: $finish called at 390 (1s)
 390 1010
```




- No, all 16 possible states are not covered here. (0000 is not covered here). Here, ring counter depends on initial state as the counter moves in loop starting from the present state. The above counter works as **Pseudo Random Sequence Generator**.

# Experiment 7

- My Entry Number is 2019MT10719 and so, I have to generate sequence 0,0,1,0,0,1.

- **State Diagram:**

 

- Here as there are 3 states, so we require at least **2 D Flip-Flops**.

- Values assigned to the states:

❖ **A = 00**

❖ **B = 01**

❖ **C = 10**

- **State Table:**

$A_n$	$B_n$	$X$	$A_{n+1}$	$B_{n+1}$	$Y$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	X	X	X
1	1	1	X	X	X

$A_n$	$B_n$	$X$	$D_A$	$D_B$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	X	X
1	1	1	X	X

- **Karnaugh Maps:**

$\begin{matrix} \text{BX} \\ \text{A} \end{matrix}$	00	01	11	10
0	0	0	1	0
1	0	0	X	X

$D_A$

$\begin{matrix} \text{BX} \\ \text{A} \end{matrix}$	00	01	11	10
0	0	1	0	0
1	0	0	X	X

$D_B$

$\begin{matrix} \text{BX} \\ \text{A} \end{matrix}$	00	01	11	10
0	0	0	0	0
1	0	1	X	X

$Y$

**Minimized Expressions are:**

- ❖  $D_A = BX$
- ❖  $D_B = A'B'X$
- ❖  $Y = AX$



- **Verilog Code:**

❖ Code for FSM :

```
module seqgenerator(A,B,Acomp,Bcomp,Y,X,clk,rst);

input clk,rst,X;
output A,B,Acomp,Bcomp,Y;
wire DA,DB;

and(DA,B,X);
and(DB,Acomp,Bcomp,X);
and(Y,A,X);

DFlipFlop DF1(A,Acomp,DA,clk,rst);
DFlipFlop DF2(B,Bcomp,DB,clk,rst);

endmodule

module DFlipFlop(Q,Qcomp,D,clk,rst);

input D,clk,rst;
output reg Q,Qcomp;

always @(clk | rst)
begin
    if(rst == 1)
        begin
            Q = 0;
            Qcomp = 1;
        end
    end
end

always @(posedge clk)
begin
    Q = D;
    Qcomp = ~Q;
end
end
```

## ❖ Tester Code:

```
module test_seqgenerator;

reg clk,rst,X;
wire A,Acomp,B,Bcomp,Y;

seqgenerator DUT(A,B,Acomp,Bcomp,Y,X,clk,rst);

always #10 clk = ~clk;

initial
begin
    $dumpfile("seqgenerator.vcd");
    $dumpvars(0,test_seqgenerator);
    $monitor ($time," A = %b, B = %b, Y = %b", A,B, Y);
    clk = 0;
    rst = 1;
    X = 1;
    #2; rst = 0;
    #30; X = 0;
    #30; X = 1;
    #30; X = 0;
    #30; X = 1;
    repeat(20) @(posedge clk);
    $finish;
end

endmodule
```

❖ Output:

```
C:\Users\Raunak\Desktop\ELL201 Verilog>vvp model
VCD info: dumpfile seqgenerator.vcd opened for output.
      0 A = 0, B = 0, Y = 0
     10 A = 0, B = 1, Y = 0
     30 A = 1, B = 0, Y = 1
     32 A = 1, B = 0, Y = 0
     50 A = 0, B = 0, Y = 0
     70 A = 0, B = 1, Y = 0
     90 A = 1, B = 0, Y = 1
     92 A = 1, B = 0, Y = 0
    110 A = 0, B = 0, Y = 0
    130 A = 0, B = 1, Y = 0
    150 A = 1, B = 0, Y = 1
    170 A = 0, B = 0, Y = 0
    190 A = 0, B = 1, Y = 0
    210 A = 1, B = 0, Y = 1
    230 A = 0, B = 0, Y = 0
    250 A = 0, B = 1, Y = 0
    270 A = 1, B = 0, Y = 1
    290 A = 0, B = 0, Y = 0
    310 A = 0, B = 1, Y = 0
    330 A = 1, B = 0, Y = 1
    350 A = 0, B = 0, Y = 0
    370 A = 0, B = 1, Y = 0
    390 A = 1, B = 0, Y = 1
    410 A = 0, B = 0, Y = 0
    430 A = 0, B = 1, Y = 0
    450 A = 1, B = 0, Y = 1
    470 A = 0, B = 0, Y = 0
    490 A = 0, B = 1, Y = 0
test_seqgenerator.v:24: $finish called at 510 (1s)
     510 A = 1, B = 0, Y = 1
```

